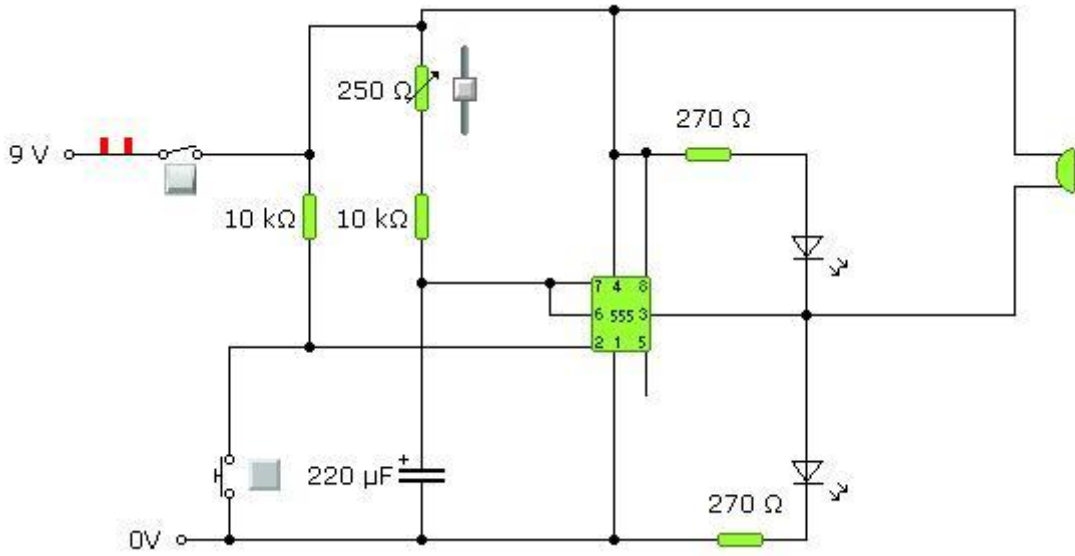


### Electronics Exercise



Identify all of the components and try to explain their purpose

.....

.....

.....

.....

.....

.....

.....

.....

.....

Explanation of how the circuit works

.....

.....

.....

.....

Name:

Form: